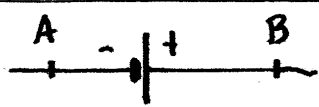





## APPLICATIONS OF LINEAR SYSTEMS

### ▼ DC circuits

- Every circuit component is associated with a voltage drop across that component. The circuit components we are interested are:

Name	Notation	$V_{AB} \equiv V_A - V_B$
Generator		$V_{AB} = -E$
Resistor		$V_{AB} = IR$
Inductor		$V_{AB} = L \frac{dI}{dt}$
Capacitor		$V_{AB} = \frac{1}{C} \int_{-\infty}^t I d\tau$

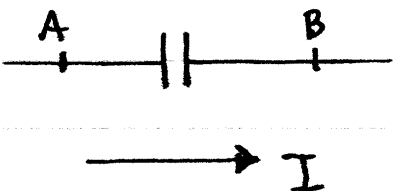$V_{AB}$  = voltage drop from A to B

$E$  = voltage of DC generator


$R$  = resistance

$L$  = inductance

$C$  = capacitance.

- Method: To calculate the currents around a circuit we work as follows.
- <sub>1</sub> Define loop currents  $I_A, I_B$ , etc. associated with each loop.
  - <sub>2</sub> For each, the sum of all of all voltage drops around the loop must be zero. Thus, for each loop, we have an equation.
  - <sub>3</sub> Solve the system of equations to find the loop currents.
  - <sub>4</sub> From the loop currents we may calculate the branch currents, voltage drops, etc.

example

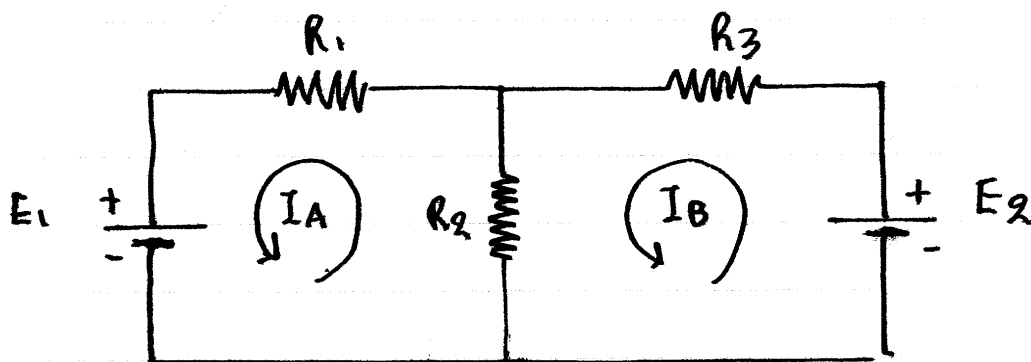

$$\begin{aligned} \text{Loop A: } & \left\{ \begin{aligned} +E_1 + I_A R_1 + (I_A - I_B) R_2 &= 0 \quad (\Leftarrow) \\ -E_2 + I_B R_3 + (I_B - I_A) R_2 &= 0 \end{aligned} \right. \\ \text{Loop B: } & \end{aligned}$$

$$\Leftrightarrow \begin{cases} (R_1 + R_2) I_A + (-R_2) I_B = -E_1 \\ (-R_2) I_A + (R_2 + R_3) I_B = E_2 \end{cases}$$

$$\Leftrightarrow \underbrace{\begin{bmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{bmatrix}}_A \begin{bmatrix} I_A \\ I_B \end{bmatrix} = \begin{bmatrix} -E_1 \\ E_2 \end{bmatrix}$$

$$\begin{aligned} \det A &= \begin{vmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{vmatrix} = \\ &= (R_1 + R_2)(R_2 + R_3) - (-R_2)^2 = \\ &= R_1 R_2 + R_1 R_2 + R_2^2 + R_2 R_3 - R_2^2 = \\ &= R_1 R_2 + R_2 R_3 + R_2 R_1 \neq 0 \\ &\text{since } R_1 > 0, R_2 > 0 \text{ and } R_3 > 0. \end{aligned}$$

Thus:

$$\begin{aligned} \begin{bmatrix} I_A \\ I_B \end{bmatrix} &= \frac{1}{\det A} \begin{bmatrix} R_2 + R_3 & +R_2 \\ +R_2 & R_1 + R_2 \end{bmatrix} \begin{bmatrix} -E_1 \\ E_2 \end{bmatrix} \\ &= \frac{1}{\det A} \begin{bmatrix} -E_1(R_2 + R_3) + E_2 R_2 \\ -E_1 R_2 + E_2(R_1 + R_2) \end{bmatrix} \end{aligned}$$

so

$$I_A = \frac{-E_1(R_2 + R_3) + E_2 R_2}{R_1 R_2 + R_2 R_3 + R_2 R_1}$$

$$I_B = \frac{-E_1 R_2 + E_2(R_1 + R_2)}{R_1 R_2 + R_2 R_3 + R_2 R_1}$$

- Current through  $R_1 : I_A$   
 $R_2 : I_A - I_B$   
 $R_3 : I_B$

- Find the necessary and sufficient condition so there is no current through  $R_2$ .

$$\text{Balance} \Leftrightarrow I_A - I_B = 0 \Leftrightarrow I_A = I_B \Leftrightarrow$$


$$\Leftrightarrow -E_1(R_2 + R_3) + E_2 R_2 = E_1 R_2 + E_2(R_1 + R_2)$$

$$\Leftrightarrow \underline{E_1 R_2} + E_1 R_3 - \underline{E_2 R_2} = \underline{E_1 R_2} - E_2 R_1 - \underline{E_2 R_2}$$


$$\Leftrightarrow E_1 R_3 = -E_2 R_1 \Leftrightarrow \boxed{E_1 = -E_2 \frac{R_1}{R_3}}$$



## EXERCISES

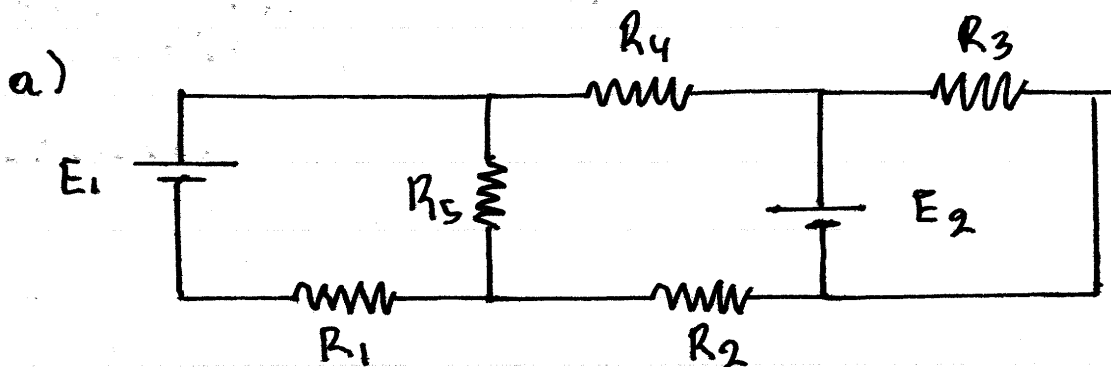(1) Find the loop currents in the following circuits.


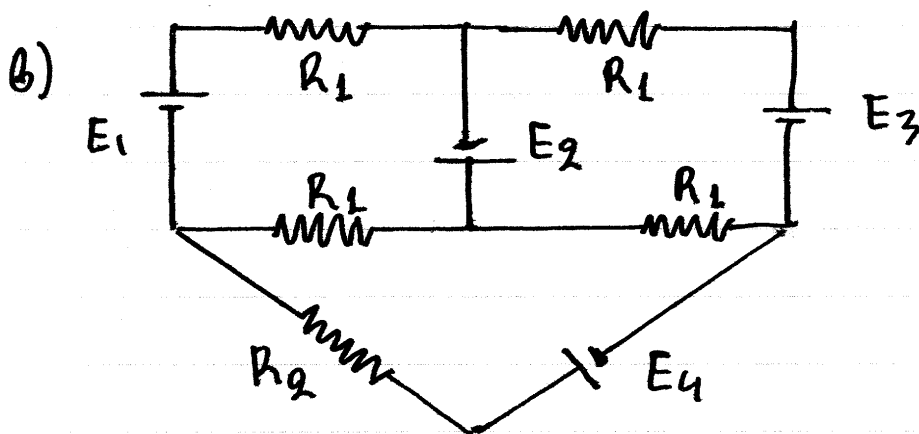
$$\text{when } R_1 = R_2 = R_3 = a$$
$$R_4 = R_5 = b$$



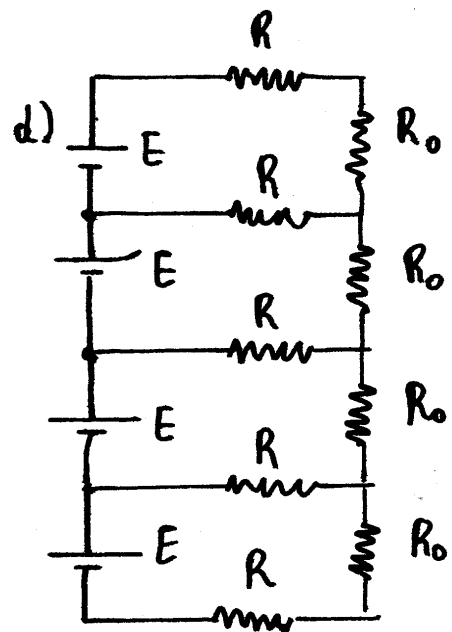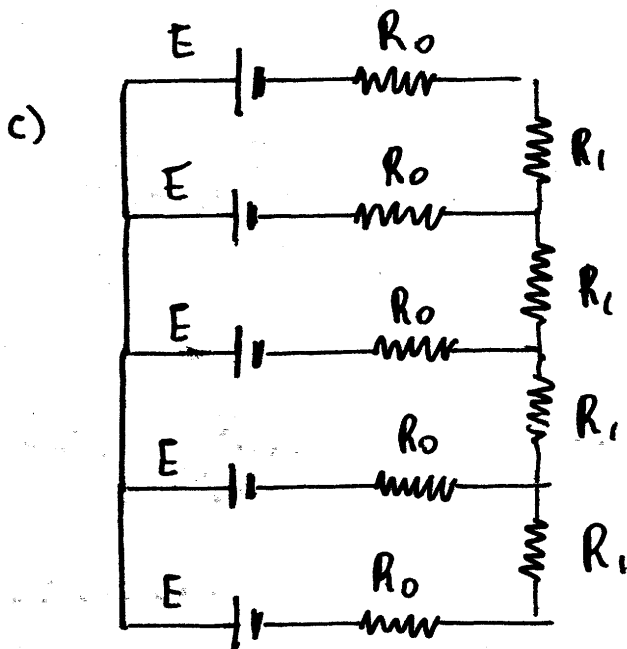


(2)

Parallel Resistors.

Show that two resistors  $R_1, R_2$  connected in parallel to a generator are equivalent to a single resistor  $R$  with

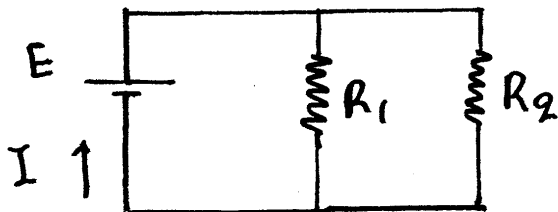
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \quad (1)$$



(i.e.  $E = IR$   
with  $R$  given  
by (1)).
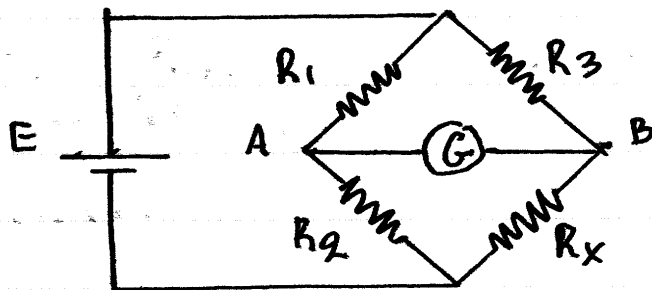
### ③ Wheatstone Bridge

The Wheatstone bridge can be used to measure the unknown resistance  $R_x$ .



ⓐ is a galvanometer measuring voltage drop  $V_{AB}$  between A and B.

Assume the Galvanometer has resistance  $R_g$ .

(a) Solve for the 3 loop currents in general.

(b) Show that when  $V_{AB} = 0$  then

$$R_x = (R_2/R_1) R_3.$$

## ↪ Superposition principle

- Any general DC circuit with  $n$  loops and  $m$  generators gives a linear system of equations of the form

$$\boxed{R \mathcal{J} = P \mathcal{E}}$$

with  $R$  the resistance matrix ( $R \in M_{nn}(\mathbb{R})$ )  
 $P$  the source configuration matrix  
( $P \in M_{nm}(\mathbb{R})$ )

and

$$\mathcal{J} = \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_n \end{bmatrix} \quad \text{and} \quad \mathcal{E} = \begin{bmatrix} E_1 \\ E_2 \\ \vdots \\ E_m \end{bmatrix}$$

- If  $R$  has an inverse then this system has a unique solution

$$\mathcal{J} = R^{-1} P \mathcal{E}$$

- Thm: Let  $\mathcal{J}_1$  be the solution when all generators are turned off except  $E_1$ , and similarly for  $\mathcal{J}_2, \mathcal{J}_3, \dots, \mathcal{J}_m$ .  
Then

$$\mathcal{J} = \mathcal{J}_1 + \mathcal{J}_2 + \dots + \mathcal{J}_m$$



## Proof

Define

$$\mathcal{E}_1 = \begin{bmatrix} \mathcal{E}_1 \\ 0 \\ \vdots \\ 0 \end{bmatrix}, \quad \mathcal{E}_2 = \begin{bmatrix} 0 \\ \mathcal{E}_2 \\ \vdots \\ 0 \end{bmatrix}, \quad \dots, \quad \mathcal{E}_m = \begin{bmatrix} 0 \\ 0 \\ \vdots \\ \mathcal{E}_m \end{bmatrix}$$

Then

$$\mathcal{E} = \mathcal{E}_1 + \mathcal{E}_2 + \dots + \mathcal{E}_m$$

For each problem we get a linear system.

Altogether:

$$\begin{cases} \mathcal{R} \mathcal{J}_1 = \mathcal{P} \mathcal{E}_1 \\ \mathcal{R} \mathcal{J}_2 = \mathcal{P} \mathcal{E}_2 \\ \vdots \\ \mathcal{R} \mathcal{J}_m = \mathcal{P} \mathcal{E}_m \end{cases} \Rightarrow \begin{cases} \mathcal{J}_1 = \mathcal{R}^{-1} \mathcal{P} \mathcal{E}_1 \\ \mathcal{J}_2 = \mathcal{R}^{-1} \mathcal{P} \mathcal{E}_2 \\ \vdots \\ \mathcal{J}_m = \mathcal{R}^{-1} \mathcal{P} \mathcal{E}_m \end{cases}$$

It follows that

$$\begin{aligned} \mathcal{J} &= \mathcal{R}^{-1} \mathcal{P} \mathcal{E} = \mathcal{R}^{-1} \mathcal{P} (\mathcal{E}_1 + \mathcal{E}_2 + \dots + \mathcal{E}_m) \\ &= \mathcal{R}^{-1} \mathcal{P} \mathcal{E}_1 + \mathcal{R}^{-1} \mathcal{P} \mathcal{E}_2 + \dots + \mathcal{R}^{-1} \mathcal{P} \mathcal{E}_m \\ &= \mathcal{J}_1 + \mathcal{J}_2 + \dots + \mathcal{J}_m. \end{aligned}$$

## ↙ Incidence Matrices

- Consider a circuit with  $n$ -loops. Define  
 $E_{ab}$  = the total generators shared by loop  $a$  and  $b$   
 $R_{ab}$  = the total resistance shared by loop  $a$  and  $b$   
 $I_a$  = the loop current for loop  $a$   
 $\delta_{ab} = \begin{cases} 1, & \text{if } a=b \\ 0, & \text{if } a \neq b. \end{cases}$

and note that  $E_{ab} = E_{ba}$  and  $R_{ab} = R_{ba}$

- Can we write  $R_{ab}$  in terms of  $R_{ab}$ ?
- Note that the equation for loop  $a$  reads:

$$\sum_b E_{ab} = \sum_{b \neq a} R_{ab} (I_a - I_b) + R_{aa} I_a$$

The right-hand-side can be rewritten as:

$$\begin{aligned} \text{RHS} &= \sum_{b \neq a} R_{ab} (I_a - I_b) + R_{aa} I_a \\ &= I_a \sum_b R_{ab} - \sum_{b \neq a} R_{ab} I_b \\ &= I_a \sum_{\gamma} R_{a\gamma} - \sum_b R_{ab} (1 - \delta_{ab}) I_b = \\ &= \sum_b \left[ \delta_{ab} \sum_{\gamma} R_{b\gamma} \right] I_b - \sum_b R_{ab} (1 - \delta_{ab}) I_b = \end{aligned}$$

$$= \sum_b \left[ \delta_{ab} \sum_y R_{by} - R_{ab} (1 - \delta_{ab}) \right] I_b =$$

$$= \sum_b R_{ab} I_b$$

therefore

$$R_{ab} = \delta_{ab} \sum_y R_{by} - R_{ab} (1 - \delta_{ab})$$

example

For  $n=2$ : two loops

$$R_{11} = \delta_{11} \sum_y R_{1y} - R_{11} (1 - \delta_{11}) = R_{11} + R_{12}$$

$$R_{12} = \delta_{12} \sum_y R_{1y} - R_{12} (1 - \delta_{12}) = -R_{12}$$

$$R_{21} = \delta_{21} \sum_y R_{2y} - R_{21} (1 - \delta_{21}) = -R_{21} = -R_{12}$$

$$R_{22} = \delta_{22} \sum_y R_{2y} - R_{22} (1 - \delta_{22}) = R_{21} + R_{22}$$

$$= R_{12} + R_{22}$$

thus  $R = \begin{bmatrix} R_{11} + R_{12} & -R_{12} \\ -R_{12} & R_{22} + R_{12} \end{bmatrix}$

- It is not always true that  $R$  has an inverse.

e.g. when  $R_{11} = 0$  and  $R_{22} = 0$   
then  $\det(R) = 0$

This situation indicates a short-circuit.

- The incidence matrix can be of use if you want to write a computer program that can solve arbitrary circuits.

### EXERCISE

- ④ Derive the relation between  $R$  and the incidence matrix  $R$  for the general  $n=3$  circuit (3 loops). Then calculate and simplify the determinant  $\det(R)$ . Under what conditions is  $R$  singular?

## Least-squares fit

- Consider a set of data points  $(x_1, y_1), (x_2, y_2), \dots, (x_n, y_n)$  that approximately fall upon a line  $(l): y = ax + b$ .
- Want to find the best possible values for  $a$  and  $b$ .

### ► Solution

Define

$$\begin{aligned} \sum x &= x_1 + x_2 + \dots + x_n \\ \sum y &= y_1 + y_2 + \dots + y_n \\ \sum x^2 &= x_1^2 + x_2^2 + \dots + x_n^2 \\ \sum y^2 &= y_1^2 + y_2^2 + \dots + y_n^2 \end{aligned}$$

$$\text{and } \sum xy = x_1y_1 + x_2y_2 + \dots + x_ny_n.$$

We estimate the error in the line fit by calculating

$$E(a, b) = \sum_{k=1}^n (y_k - (ax_k + b))^2$$

To minimize  $E(a, b)$  we calculate the partial derivatives with respect to  $a$  and  $b$ :

$$\begin{aligned}
\frac{\partial E(a,b)}{\partial a} &= \frac{\partial}{\partial a} \sum_{k=1}^n [y_k - (ax_k + b)]^2 = \\
&= \sum_{k=1}^n \left\{ \frac{\partial}{\partial a} [y_k - (ax_k + b)]^2 \right\} = \\
&= \sum_{k=1}^n \left\{ 2[y_k - (ax_k + b)](-x_k) \right\} = \\
&= \sum_{k=1}^n [-2x_k y_k + 2ax_k^2 + 2bx_k] \\
&= -2 \sum_{k=1}^n x_k y_k + 2a \sum_{k=1}^n x_k^2 + 2b \sum_{k=1}^n x_k \\
&= -2 S_{xy} + 2a S_{xx} + 2b S_x
\end{aligned}$$

and

$$\begin{aligned}
\frac{\partial E(a,b)}{\partial b} &= \frac{\partial}{\partial b} \sum_{k=1}^n [y_k - (ax_k + b)]^2 = \\
&= \sum_{k=1}^n \left\{ \frac{\partial}{\partial b} [y_k - (ax_k + b)]^2 \right\} = \\
&= \sum_{k=1}^n \left\{ 2[y_k - (ax_k + b)](-1) \right\} = \\
&= \sum_{k=1}^n [-2y_k + 2ax_k + 2b] \\
&= -2 \sum_{k=1}^n y_k + 2a \sum_{k=1}^n x_k + 2nb \\
&= -2 S_y + 2a S_x + 2nb
\end{aligned}$$

At the minimum we have

$$\begin{cases} \frac{\partial E(a,b)}{\partial a} = 0 \\ \frac{\partial E(a,b)}{\partial b} = 0 \end{cases} \Leftrightarrow \begin{cases} -2 \sum_{xy} + 2a \sum_{xx} + 2b \sum_x = 0 \\ -2 \sum_y + 2a \sum_x + 2nb = 0 \end{cases}$$

$$\Leftrightarrow \begin{bmatrix} \sum_{xx} & \sum_x \\ \sum_x & n \end{bmatrix} \begin{bmatrix} a \\ b \end{bmatrix} = \begin{bmatrix} \sum_{xy} \\ \sum_y \end{bmatrix}$$

$$D_a = \begin{vmatrix} \sum_{xx} & \sum_x \\ \sum_x & n \end{vmatrix} = n \sum_{xx} - [\sum_x]^2$$

$$D_a = \begin{vmatrix} \sum_{xy} & \sum_x \\ \sum_y & n \end{vmatrix} = n \sum_{xy} - \sum_x \sum_y$$

$$D_b = \begin{vmatrix} \sum_{xx} & \sum_{xy} \\ \sum_x & \sum_y \end{vmatrix} = \sum_{xx} \sum_y - \sum_{xy} \sum_x$$

consequently,

$$a = \frac{n \sum_{xy} - \sum_x \sum_y}{n \sum_{xx} - [\sum_x]^2}$$

$$b = \frac{\sum_{xx} \sum_y - \sum_{xy} \sum_x}{n \sum_{xx} - [\sum_x]^2}$$

- Will we always have  $D = n \sum x_k^2 - [\sum x_k]^2 \neq 0$ ?

Answer: We use the Lagrange identity:

$$\begin{aligned} & \left( \sum_{k=1}^n a_k^2 \right) \left( \sum_{k=1}^n b_k^2 \right) - \left( \sum_{k=1}^n a_k b_k \right)^2 = \\ & = \frac{1}{2} \sum_{k=1}^n \sum_{l=1}^n \begin{vmatrix} a_k & b_k \\ a_l & b_l \end{vmatrix}^2 \end{aligned}$$

It follows that

$$\begin{aligned} D &= n \sum x_k^2 - [\sum x_k]^2 = \\ &= (1^2 + 1^2 + \dots + 1^2) (x_1^2 + x_2^2 + \dots + x_n^2) - \\ & \quad (1x_1 + 1x_2 + \dots + 1x_n)^2 = \\ &= \frac{1}{2} \sum_{k=1}^n \sum_{l=1}^n \begin{vmatrix} 1 & x_k \\ 1 & x_l \end{vmatrix}^2 = \\ &= \frac{1}{2} \sum_{k=1}^n \sum_{l=1}^n (x_k - x_l)^2 \geq 0 \end{aligned}$$

As long as at least two of  $x_1, x_2, \dots, x_n$  are not equal to each other, we see that  $D > 0 \Rightarrow D \neq 0$ .



- How do we know that the solution we found is really a minimum and not a maximum?

Answer: A sufficient condition for a minimum is that

$$\frac{\partial^2 E(a,b)}{\partial a^2} > 0 \quad (1), \text{ and}$$

$$M(a,b) = \frac{\partial^2 E(a,b)}{\partial a^2} \frac{\partial^2 E(a,b)}{\partial b^2} - \left[ \frac{\partial^2 E(a,b)}{\partial a \partial b} \right]^2 > 0 \quad (2)$$

(1)  $\rightarrow$  minimum in a direction

(2)  $\rightarrow$  same curvature in all directions.

Recall that

$$\frac{\partial E(a,b)}{\partial a} = -2 \zeta_{xy} + 2a \zeta'_{xx} + 2b \zeta'_x$$

$$\frac{\partial E(a,b)}{\partial b} = -2 \zeta_y + 2a \zeta'_x + 2nb$$

It follows that

$$\frac{\partial^2 E(a,b)}{\partial a^2} = 2 \zeta'_{xx}, \quad \frac{\partial^2 E(a,b)}{\partial b^2} = 2n, \text{ and}$$

$$\frac{\partial^2 E(a,b)}{\partial a \partial b} = 2 \zeta'_x$$

and thus for eq. (1):

$$\frac{\partial^2 E(a,b)}{\partial a^2} = 2 \sum_{xx} = 2 \sum_{k=1}^n x_k^2 > 0$$

if at least one  $x_k \neq 0$ .

$$M(a,b) = (2 \sum_{xx})(2n) - (2 \sum_x)^2 =$$

$$!!! \left( = 4(n \sum_{xx} - (\sum_x)^2) \right)$$

$$= 4D > 0 \leftarrow \text{if at least one } x_k - x_l \neq 0 \text{ for } k \neq l.$$

► Note the amusing relationship between  $M(a,b)$  and the determinant  $D$ !!

## EXERCISES

⑤ Find the least-square fit line given the data

a)  $(-1, -2), (0, 0), (1, 2 + \Delta 2)$

b)  $(0, 0), (1, 1), (2, 2 + \epsilon)$

c)  $(1, 1), (a, a), (2, 2 + a)$

⑥ Confirm that given two data points  $(x_1, y_1)$  and  $(x_2, y_2)$  the least-square fit line corresponds to the line that does in fact go through the two data points (i.e. you have a perfect fit). You will find

$$a = \frac{y_1 - y_2}{x_1 - x_2} \quad \leftarrow \text{slope}$$

$$b = y_1 - ax_1$$

which corresponds to the line

$$(l): y - y_1 = a(x - x_1)$$

⑦ Suppose that your data points are not exact and you are given instead

$$(x_k \pm \sigma_{x_k}, y_k \pm \sigma_{y_k}), \quad k = 1, 2, 3, \dots, n$$

You may still calculate  $a, b$  as usual but because your data is not exact there will be some error in your predicted  $a$  and  $b$ . So we want  $a \pm \sigma_a$ , and  $b \pm \sigma_b$ .

It can be shown that

$$\sigma_a^2 = \sum_{k=1}^n \left( \frac{\partial a}{\partial x_k} \right)^2 \sigma_{x_k}^2 + \sum_{k=1}^n \left( \frac{\partial a}{\partial y_k} \right)^2 \sigma_{y_k}^2$$

$$\sigma_b^2 = \sum_{k=1}^n \left( \frac{\partial b}{\partial x_k} \right)^2 \sigma_{x_k}^2 + \sum_{k=1}^n \left( \frac{\partial b}{\partial y_k} \right)^2 \sigma_{y_k}^2$$

Calculate the derivatives

$$\frac{\partial a}{\partial x_k}, \frac{\partial a}{\partial y_k}, \frac{\partial b}{\partial x_k}, \frac{\partial b}{\partial y_k}$$

↑  
→ Obviously, given these derivatives we can write a computer program that finds  $\sigma_a$  and  $\sigma_b$  in addition to  $a$  and  $b$  from the data.